

**Figure 1.** Pictorial explanations of cancellation method used in MOS multipliers. (a) Using single-quadrant multipliers and (b) using square devices correspond to Eqs. (1) and (2) respectively.  $X$  and  $Y$  are not shown in the figures for simplicity.

**OPERATION PRINCIPLES**

Despite many reported MOS multipliers, only two cancellation methods for the four-quadrant multiplication are known. A fully differential configuration is necessary in a sound multiplier topology to achieve complete cancellation. As a multiplier has two inputs, there are four combinations of two differential signals, i.e.,  $(x, y)$ ,  $(-x, y)$ ,  $(-x, -y)$ , and  $(x, -y)$ . Then, the multiplication can be obtained based on the following equalities.

$$\begin{aligned} & [(X + x)(Y + y) + (X - x)(Y - y)] \\ & - [(X - x)(Y + y) + (X + x)(Y - y)] = 4xy \end{aligned} \tag{1}$$

or

$$\begin{aligned} & [ \{ (X + x) + (Y + y) \}^2 + \{ (X - x) + (Y - y) \}^2 ] \\ & - [ \{ (X - x) + (Y + y) \}^2 + \{ (X + x) + (Y - y) \}^2 ] = 8xy \end{aligned} \tag{2}$$


$X$  and  $Y$  are constant terms that include a common mode signal, and any constant terms in device characteristics. Figure 1 depicts an explanation of the above equations. The simple MOS transistor model expressed for its linear and saturation regions, as

$$I_d = K \left[ V_{gs} - V_t - \frac{V_{ds}}{2} \right] V_{ds} = K \left[ V_{gs} V_{ds} - V_t V_{ds} - \frac{V_{ds}^2}{2} \right] \tag{3}$$

for  $|V_{gs}| > |V_t|, |V_{ds}| < |V_{gs} - V_t|$

$$I_d = \frac{K}{2} [V_{gs} - V_t]^2 = \frac{K}{2} [V_{gs}^2 - 2V_{gs}V_t - V_t^2] \tag{4}$$


for  $|V_{gs}| > |V_t|, |V_{ds}| > |V_{gs} - V_t|$

 

**Figure 2.** Programmable transconductor (one-quadrant multiplier).  $M_1$  is operating in linear region while  $M_2$  is operating in saturation region.

**MULTIPLIERS, ANALOG CMOS**

Multipliers produce linear products of two signals  $x$  and  $y$  yielding an output  $z = Kxy$ , where  $K$  is a multiplication constant with suitable dimension. Historically, a complete analog multiplier was invented by Gilbert (1,2) using BJT. Because digital technology dominates in modern electronics, analog circuits are required to share the same standard digital CMOS process for low cost fabrication. Thus, the popular BJT Gilbert Cell is not suitable in an MOS digital process, and designers must address low power supply voltage requirements. The Gilbert cell is implemented using lateral BJT in the CMOS process in Ref. 3. The MOS version of Gilbert multipliers is reported in Ref. 4. Because its linearity is poor, several modified versions including linearization schemes (4–6), folded structures (6–8), and active attenuators (9) have been reported. However, none of the above multipliers has been adopted in any commercial product. Many other MOS multipliers that are not based on Gilbert cell structure are reported in the literature. MOS multipliers can be categorized into two major groups based on its MOS operating region, linear (10–25) and saturation (3–9,26–48). Beside above major categories multipliers operating in the weak inversion region (49–51), dynamic multipliers for sampled signal system or neural networks (52–57), has been reported. Here, only the MOS multiplier architectures that have practical performance are discussed.

 


**Figure 3.** Four-quadrant multipliers with two programmable transconductors.

where  $K = \mu_0 C_{ox} W/L$  and  $V_t$  are the conventional notation for the transconductance parameter and the threshold voltage of the MOS transistor, respectively. The terms  $V_{gs} V_{ds}$  in Eq. (3), or  $V_{gs}^2$  in Eq. (4) are commonly used to implement Eqs. (1) and (2), respectively.

**Using  $V_{gs} V_{ds}$  in Linear Region**

First we introduce a programmable linear transconductor and show how it can be used to implement a multiplier. In Fig. 2, transistor  $M_1$  is forced to operate in the linear region while  $M_2$  operates in saturation with proper bias voltage,  $X$  and  $Y$ . In Fig. 2(a) (58),  $v_{ds,M_1}$  is controlled by  $y$  through the source follower  $M_2$  when the transconductance of the source follower

 

**Figure 5.** Four cross coupled FETs with gate and source signal application.

is much larger than that of  $M_1$ . The source follower can be replaced with the BJT emitter follower (59) [Fig. 2(b)] or the gain enhanced MOS source follower (60–62).


A multiplier is realized by combining two programmable transconductors as shown in Fig. 3(a). The output current is obtained from Eq. (3) where  $X \pm x = v_{gs}$  and  $y = v_{ds}$ .

$$\begin{cases} I_1 = K_1 \left( X + x - V_t - \frac{y}{2} \right) y \\ I_2 = K_1 \left( X - x - V_t - \frac{y}{2} \right) y \end{cases} \quad (5)$$


The difference of output currents yields

$$I_o = I_1 - I_2 = 2K_1xy \quad (6)$$

In Fig. 3(a), the op amp keeps the sources of the FETs virtually grounded. This approach has been used in conjunction with switched-capacitor circuits to implement a weighted-sum

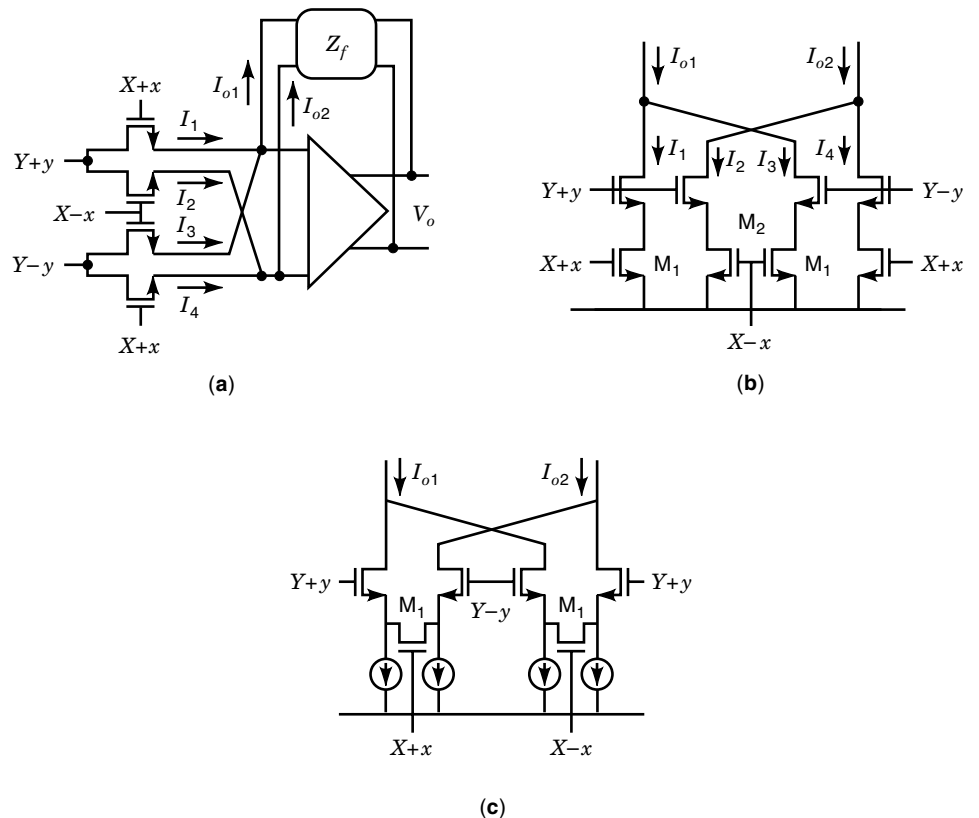

**Figure 4.** Fully-differential four-quadrant multipliers using  $V_{gs} V_{ds}$  term.

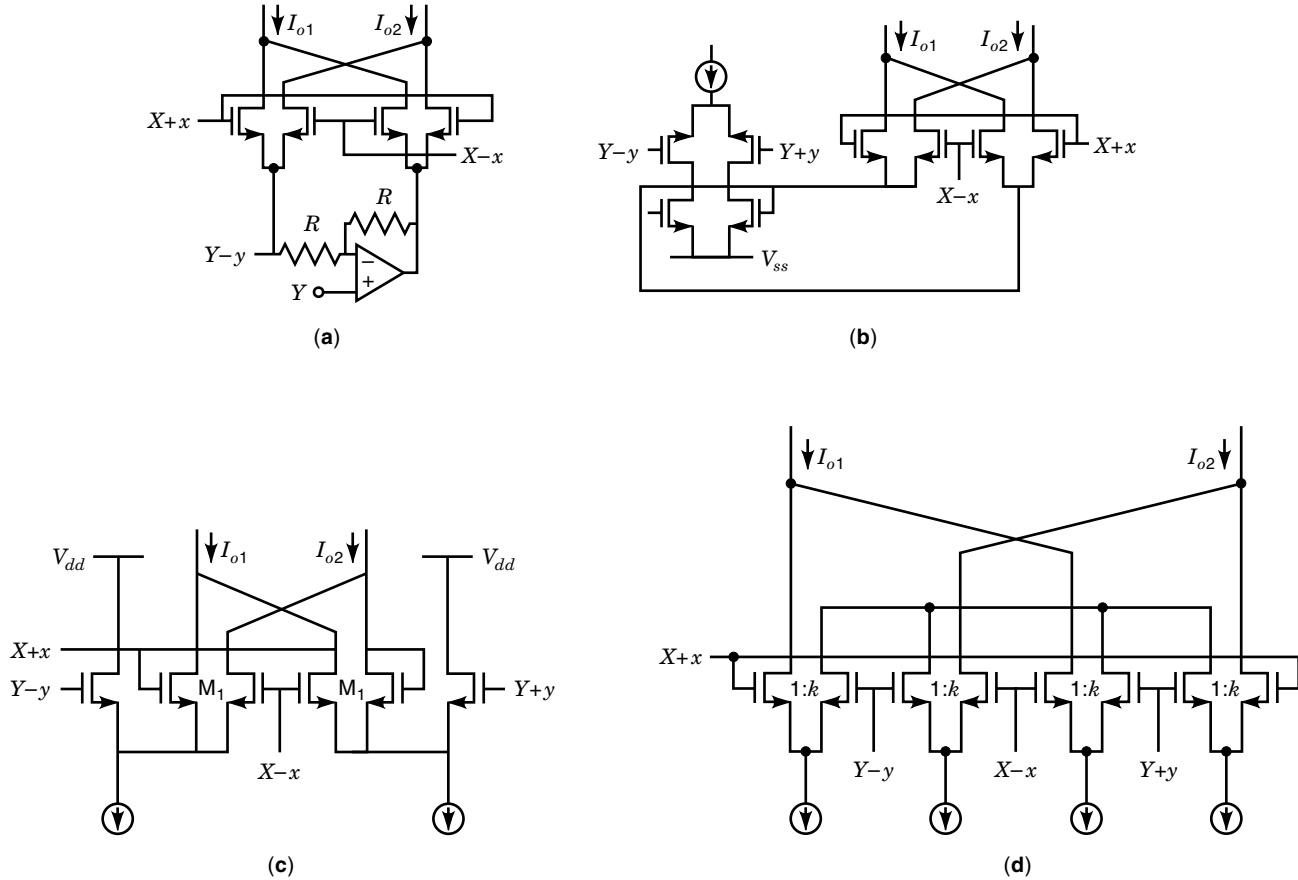

**Figure 6.** Source signal injection methods for multiplier using  $v_{gs}^2$  term.


or a weighted-integrator (9–12). The configuration in Fig. 3(b) uses MOS source followers and achieves multiplication as in Eq. (5) except  $y$  in Eq. (5) is replaced with  $Y \pm y - V_t$ . This configuration is reported in (13–17) with gain enhanced source follower.

A fully differential extension shown in Fig. 4 achieves complete common mode and power supply dependency cancellation and yields

$$I_o = I_{o1} - I_{o2} = (I_1 + I_3) - (I_2 + I_4) = 4K_1xy \quad (7)$$

or

$$V_o = -Z_f I_o = -4K_1 Z_f xy \quad (8)$$

 

**Figure 7.** Multiplier that utilizes  $V_{gs}^2$  using voltage adder.  $\oplus$  represents voltage adder circuit.

The variations of Fig. 4(a) are reported in Refs. 18–21 and the circuit in Fig. 4(b) is reported in Ref. 22. The  $V_{ds}$  of  $M_1$ , which is operating in linear region, also can be applied by two source followers as shown in Fig. 4(c) (23,24).

#### Using $V_{gs}^2$ with Gate and Source Injection


A four-quadrant multiplier based on the topology in Fig. 1(b) can be realized by four cross-coupled transistors as shown in Fig. 5 whose output current,  $I_o$ , is

$$I_o = I_{o1} - I_{o2} = 4Kxy \quad (9)$$

Varieties of source signal application methods are reported in the literature. Figure 6(a) uses an op-amp (26), (b) uses a linear differential amplifier (27), and (c) uses source followers. A separate source follower, as shown in Fig. 6(d) (28), can be provided to each transistor in cross-coupled transistors. A gain-enhanced source follower (29–34) or a BJT buffer (35) can be used to apply the source signal. This type is the most widely implemented multiplier structure.

#### Using $V_{gs}^2$ with Voltage Adder

Another way to utilize the  $V_{gs}^2$  term of MOS transistor operating in saturation region is to apply the sum or difference of two input signals to the gate of MOS transistor while the source voltage is fixed, as shown in Fig. 7(a). This configuration is reported in (36–38) using a capacitive adder, in Ref. 39 using resistive adder, in Refs. 40–43 using an active adder,

 

**Figure 8.** Simulated total harmonic distortion for  $W/L = 10 \mu\text{m}/10 \mu\text{m}$  for all transistor. The  $X$  and  $Y$  are set to allow  $IV$  input range for  $x, y$ . (a)  $2x = 1$  V; (b)  $2y = 1$  V.

and in Refs. 44–46 using programmable floating voltage source. This type has the following output:

$$I_o = 4KK_a xy \quad (10)$$

where  $K_a$  is the gain of the voltage summing circuit and  $K$  is the transconductance coefficient as usual. Reference 47 provides a summary of this multiplier type.

#### REMARKS ON MULTIPLIER STRUCTURES

None of the above analyses includes higher order effects such as the  $\gamma$ -effect,  $\lambda$ -effect, and mobility degradation effect. These effects are more severe in short channel devices. Besides the higher order effect of MOS in the multiplier core, the nonidealities of the source follower and voltage adder were not considered. Another practical limitation of the multiplier is the component mismatch that causes nonlinearity and offset.

The measurements of multiplier performance can include input range, linearity, common mode effects, minimum power supply voltage, power consumption, silicon area, frequency range noise, and so on. Since all these performance measures are strongly design dependent there is not an absolute standard comparison metric. However, the circuits in Fig. 4(a), Fig. 6(a), and Fig. 7 require additional circuitry and there is no clear theoretical advantage. These circuits are not discussed further in this article. Following detailed analysis for the rest of circuits will suggest the most recommended analog MOS multiplier structure.

**Linearity.** The linearity simulation result in Fig. 8 shows that circuit Fig. 4(c) and Fig. 6(d) have poor linearity. The performances of the circuits in Fig. 4(b) and Fig. 6(c) are strongly dependent on the ideality of source follower. Figure 9 shows that the linearity of circuit Fig. 4(b) improves as the source follower uses larger  $W/L$  ratio. On the contrary, this effect is not clear for circuit Fig. 6(c). This result implies that circuit Fig. 4(b) can outperform circuit Fig. 6(c) when  $K_2$  is large enough (at least three times larger than  $K_1$ ). Although the simulated linearity in Fig. 8 of the circuit Fig. 6(b) is comparable with others, Monte Carlo analysis reveals that high sensitivity to process variation causes poor linearity.

Figure 10 shows the linearity error measured from the fabricated multiplier using Orbit  $2\mu\text{m}$  N-well process. These


multipliers were designed with identical transistor size [ $(W/L)_1 = 4 \mu\text{m}/17 \mu\text{m}$  and  $50 \mu\text{m}/10 \mu\text{m}$  for all others], transconductance, power consumption ( $360 \mu\text{W}$ ), and input range ( $\pm 2$  V differential input range for both  $x$  and  $y$ ). The linearity error of the circuit Fig. 4(b) is lower than 0.5%. It is much better than the other because the  $W/L$  ratio of the source follower is much larger than that of  $M_1$ . These results agree well with the simulation results discussed above.

**Input Range and Minimum Power Supply Voltage.** Input ranges of circuits Fig. 4(b) and Fig. 6(c) are obtained from their bias conditions shown in Fig. 11. The conditions for circuit Fig. 4(b) are


$$\begin{cases} V_t < X \pm x \\ V_1 = Y \pm y - V_t < X \pm x - V_t \\ V_t < Y \pm y \\ Y \pm y - V_t < V_d \end{cases} \quad (11)$$

These conditions are depicted in Fig. 12(a). The conditions for circuit Fig. 6(c) are

$$\begin{cases} V_{\text{dssat}} < V_1 = Y \pm y - V_t \\ V_1 + V_t = Y \pm y < X \pm x \\ X \pm x - V_t < V_d \end{cases} \quad (12)$$

 

**Figure 9.** The effect of source follower transistor  $W/L$  ratio on THD. The length of the source follower is fixed to  $10 \mu\text{m}$ . All other transistors have  $W/L = 10 \mu\text{m}/10 \mu\text{m}$ . The linearity of circuit Fig. 4(b) improves as the source follower uses larger  $W/L$  ratio.

 

**Figure 10.** Measured linearity error from a fabricated chip.  $(W/L)_1 = 5 \mu\text{m}/17 \mu\text{m}$  and  $(W/L)_2 = 50 \mu\text{m}/10 \mu\text{m}$ . For simplicity, only one quadrant is shown. (a) Linearity error for fixed  $y$ ; (b) Linearity error for fixed  $x$ .

These conditions are depicted in Fig. 12(b). For the same input range and output node voltage swing,  $V_o$ , circuit Fig. 4(b) requires much lower power supply voltage than Fig. 6(c).

**Noise.** Another performance measure of a multiplier is noise, especially for small signal applications where the input range is not a major concern. A thermal noise current power density of a MOS transistor is conventionally modeled as

$$\begin{cases} \overline{i_{n:\text{lin}}^2} = 4kTg_{\text{ds}}df \\ \overline{i_{n:\text{sat}}^2} = \frac{8}{3}kTg_{\text{m}}df \end{cases} \quad (13)$$


for transistor operating in linear and saturation, respectively. In the case of circuit Fig. 4(b), total output noise current is given

$$\begin{aligned} \overline{i_{n:o}^2} &= 4(\overline{i_{n:\text{lin}}^2} + \overline{i_{n:\text{sat}}^2}) = 4\left(4kTg_{\text{ds1}}df + \frac{8}{3}kTg_{\text{m2}}df\right) \\ &= 16kT\left(g_{\text{ds1}} + \frac{2}{3}g_{\text{m2}}\right)df \end{aligned} \quad (14)$$

where

$$\begin{aligned} g_{\text{ds1}} &= K_1(V_{\text{GS1}} - V_t - V_{\text{DS1}}) \\ &= K_1(X - V_t - (Y - V_t)) = K_1(X - Y) \end{aligned} \quad (15)$$

$$g_{\text{m2}} = \sqrt{2K_2I_{\text{DQ}}} = \sqrt{2K_2K_1\left(X - V_t - \frac{Y - V_t}{2}\right)(Y - V_t)} \quad (16)$$

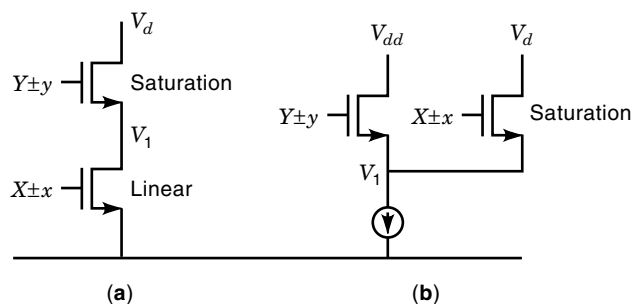

**Figure 11.** Bias conditions. (a) Circuit Fig. 4(b); (b) Circuit Fig. 6(c).


In the case of the circuit in Fig. 6(c), if the current source has the same transistor size as the source follower, then the total output noise current is given

$$\overline{i_{n:o}^2} = 4(\overline{i_{n:\text{M2}}^2} + \overline{i_{n:\text{M1}}^2}) = 4 \cdot \frac{8}{3}kT(g_{\text{m2}} + g_{\text{m1}})df \quad (17)$$

As  $g_{\text{m1}}$  in Eq. (17) is much larger than  $g_{\text{ds1}}$  in Eq. (14), the circuit in Fig. 6(c) has higher output noise. The output noise floors of fabricated multipliers are measured with 1 K $\Omega$  resistor at 1 KHz. The circuit in Fig. 4(b) shows 26 dB lower noise floor than the circuit in Fig. 6(c).

#### DESIGN ISSUES OF THE CIRCUIT IN FIG. 4(b)

Table 1 summarizes the above comparisons and proposes that the circuit in Fig. 4(b) is the most suitable analog CMOS multiplier structure. The circuit in Fig. 4(b) has a clear tradeoff

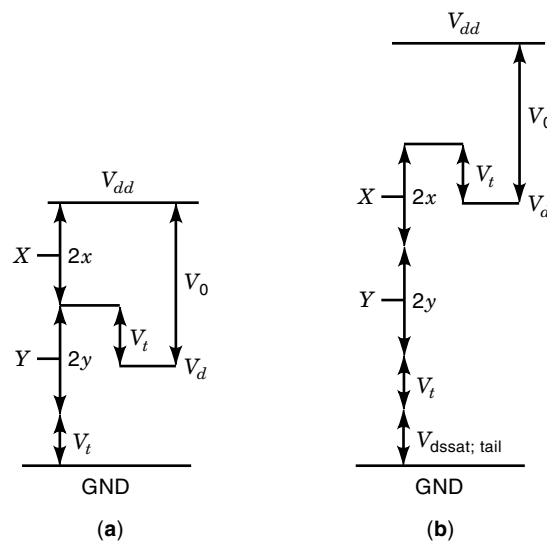

**Figure 12.** Input range and power supply voltage. When input range is 1 V for both  $x$  and  $y$ , threshold voltage  $V_t = 1 \text{ V}$ , and output signal swing is 2 V, the minimum power supply voltages are 3 and 4 V, respectively for the circuits in Fig. 4(b) and Fig. 6(c). (a) Circuit Fig. 4(b); (b) Circuit Fig. 6(c).

**Table 1. Summary of Comparisons<sup>a</sup>**

Circuit	Operating Region	Complexity	Linearity	Sensitivity	Minimum Power Supply	Noise	
Fig. 4(a)	Linear	bad					
Fig. 4(b)							
Fig. 4(c)			bad				
Fig. 6(a)	Saturation	bad					
Fig. 6(b)				bad			
Fig. 6(c)					bad	bad	
Fig. 6(d)			bad				
Fig. 7(a)		bad					
Fig. 7(b)		bad					

<sup>a</sup> Gray areas were not analyzed because circuit had already shown poor performance.

between noise and linearity. The input reflected equivalent noise voltage of the circuit in Fig. 4(b) is obtained by dividing Eq. (14) by the square of transconductance of multiplier,  $G_m$ , which is determined by  $K_1$  as in Eq. (7), yielding

$$\overline{v_{n:i}^2} = \frac{\overline{i_{n:o}^2}}{G_m^2} = \frac{\overline{i_{n:o}^2}}{16K_1^2} = \frac{kT}{K_1^2} \left( g_{ds1} + \frac{2}{3} g_{m2} \right) df \quad (18)$$

when other input is unity. Substituting  $g_{ds1}$  and  $g_{m2}$  in Eq. (18) with Eqs. (15) and (16) results in

$$\overline{v_{n:i}^2} = \frac{kT}{K_1} \left( (X - Y) + \frac{2}{3} \sqrt{2 \frac{K_2}{K_1} \left( X - \frac{Y + V_t}{2} \right) (Y - V_t)} \right) df \quad (19)$$

This analysis suggests that  $(X - Y)$  and  $K_2/K_1$  should be reduced to improve the noise performance for given  $K_1$ . This is the direct tradeoff with linearity and input range because  $K_2/K_1$  should be increased to improve linearity as illustrated in Fig. 9 and  $(X - Y)$  determines the input range as shown in Fig. 12(a).

Figure 13 shows the noise simulation result. The output noise is a linear function of  $K_1$  as in Eqs. (14)–(16). When the source follower's transconductance is large enough  $[(W/L)_2 = 20]$ , the input reflected noise is inversely proportional to  $(W/L)_1$  as in Eq. (19) because Eq. (19) is based on the assumption that the source follower is an ideal one. If the source follower is not large enough  $[(W/L)_2 = 10]$ , Eq. (19) is no longer valid, as shown in Fig. 13(b). The noise performance begins to degrade when  $K_2/K_1$  ratio is smaller than 3  $[(W/L)_2 = 10$  and  $(W/L)_1 = 3]$ . Figure 14 shows the noise dependency on source follower size and suggests that the  $K_2/K_1$  ratio

should be larger than 3. These analyses lead to two conflicting observations as follows:

1. From Fig. 13(b) and Fig. 14, the  $K_2/K_1$  ratio should be larger than 3 to make Eq. (19) valid.
2. From Eq. (19), the  $K_2/K_1$  ratio should be minimized for low input reflected noise.



These two observations lead us to the conclusion that the optimal  $K_2/K_1$  ratio for low noise design is around 3 in this specific process. Note that the  $K_2/K_1$  ratio should be maximized for high linearity.

Figure 15 shows that the input noise is almost a linear function of the difference of two input common-mode voltages,  $(X - Y)$ , as expected in Eq. (19). This difference is equivalent to the summation over half of the input range. Therefore, for low noise design, the input range should be minimized.


In designing the circuit Fig. 4(b),  $K_2/K_1$  ratio  $(X - Y)$  are key design parameters that determine the direct tradeoffs among noise, linearity and input range.

## CONCLUSION


Although a large number of MOS transconductance multipliers are reported in the literature only few practical MOS multiplier structures are discussed here. As the current trend of circuit design is low voltage and low power, the circuit shown in Fig. 4(b) seems to be one of the most attractive low voltage and high performance MOS transconductance multipliers. A BiCMOS version that uses BJT instead of source follower, or a careful design, will improve its performance further.

  

**Figure 13.** Noise dependency on  $W_1$ .  $L_{1,2} = 10 \mu\text{m}$ ,  $(X + Y)/2 = 4 \text{ V}$  and  $X - Y = 2 \text{ V}$ . The output noise is measured at the one of the output node with  $50 \Omega$  load resistor and integrated within  $1 \text{ MHz} \sim 2 \text{ MHz}$  range. (a) Output noise. The output noise is almost a linear function of  $W_1$ . (b) Input reflected noise. Input reflected equivalent noise is inversely proportional to  $W_1$ .

 

**Figure 14.** Input noise dependency on  $(W/L)_2$ :  $(W/L)_1 = 10 \mu\text{m}/10 \mu\text{m}$ ,  $V_{\text{com}} = (X + Y)/2 = 4 \text{ V}$  and  $X - Y = 2 \text{ V}$ .  $(W/L)_2$  should be larger than 3 for low noise design.

 

**Figure 15.** Noise dependency on  $(X - Y)$  for  $L = 10 \mu\text{m}$ ,  $W_1 = 10 \mu\text{m}$ ,  $W_2 = 200 \mu\text{m}$  and  $V_{\text{com}} = 4 \text{ V}$ . Input reflected noise is a linear function of input range,  $(X - Y)$ .

The reader should be aware that this conclusion might not hold for all cases. The choice of circuit topology is completely dependent on design specifications. The reader also should note that, in general, a BJT multiplier outperforms any MOS multipliers and no commercial discrete MOS multiplier has been produced.

#### BIBLIOGRAPHY

1. B. Gilbert, A precision four-quadrant multiplier with subnanosecond response, *IEEE J. Solid-State Circuits*, **SC-3**: 353–365, 1968.
2. B. Gilbert, A high-performance monolithic multiplier using active feedback, *IEEE J. Solid-State Circuits*, **SC-9**: 364–373, 1974.
3. Z. Hong and H. Melchior, Four-quadrant multiplier core with lateral bipolar transistor in CMOS technology, *Electron. Lett.*, **21**: 72–73, 1985.
4. J. N. Babanezhad and G. C. Temes, A 20-V four-quadrant CMOS analog multiplier, *IEEE J. Solid-State Circuits*, **SC-20**: 1158–1168, 1985.
5. D. C. Soo and R. G. Meyer, A four-quadrant NMOS analog multiplier, *IEEE J. Solid-State Circuits*, **SC-17**: 1174–1178, 1982.
6. S. L. Wong, N. Kalyanasundaram, and C. A. T. Salama, Wide dynamic range four-quadrant CMOS analog multiplier using linearized transconductance stage, *IEEE J. Solid-State Circuits*, **SC-21**: 1120–1122, 1986.
7. R. Tawel, R. Benson, and A. P. Thakoor, A CMOS UV-programmable non-volatile synaptic array, *Proc. IEEE Int. J. Conf. Neural Netw.*, Seattle, Vol. 1, 1991, pp. 581–585.
8. J. Ramírez and S. Ming-Shen, The folded Gilbert cell: A low voltage high performance CMOS multiplier, *Proc. IEEE Midwest Symp. Circuits Syst.*, 1992, pp. 20–23.
9. S. C. Qin and R. L. Geiger, A  $\pm 5 \text{ V}$  CMOS analog multiplier, *IEEE J. Solid-State Circuits*, **SC-22**: 1143–1146, 1987.
10. T. Enomoto and M. A. Yasumoto, Integrated MOS four-quadrant analog multiplier using switched capacitor technology for analog signal processor ICs, *IEEE J. Solid-State Circuits*, **SC-20**: 852–859, 1985.
11. Z. Zhang, X. Dong, and Z. Zhang, A single D-FET 4QAM with SC Technology, *IEEE Trans. Circuits Syst.*, **35**: 1551–1552, 1988.
12. O. Changyue, C. Peng, and Xie Yizhong, Study of switched capacitor multiplier, *Int. Conf. Circuits Syst.*, China, pp. 234–237, 1991.

13. M. Ismail et al., A configurable CMOS multiplier/divider for analog VLSI, *Proc. IEEE Int. Symp. Circuits Syst.*, 1993, pp. 1085–1088.
14. A. L. Coban and P. E. Allen, Low-voltage CMOS transconductance cell based on parallel operation of triode and saturation transconductors, *Electron. Lett.*, **30**: 1124–1126, 1994.
15. A. L. Coban and P. E. Allen, Low-voltage four-quadrant analogue CMOS multiplier, *Electron. Lett.*, **30**: 1044–1045, 1994.
16. A. L. Coban and P. Allen, A 1.5V four quadrant analog multiplier, *Proc. 37th Midwest Symp. Circuits Syst.*, Lafayette, Vol. 1, 1994, pp. 117–120.
17. A. L. Coban, P. E. Allen, and X. Shi, Low-voltage analog IC design in CMOS technology, *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, **42**: 955–958, 1995.
18. J. L. Pennock, CMOS triode transconductor for continuous-time active integrated filters, *Electron. Lett.*, **21**: 817–818, 1985.
19. N. Khachab and M. Ismail, MOS multiplier divider cell for analog VLSI, *Electron. Lett.*, **25**: 1550–1552, 1989.
20. N. Khachab and M. Ismail, A nonlinear CMOS analog cell for VLSI signal and information processing, *IEEE J. Solid-State Circuits*, **26**: 1689–1694, 1991.
21. S. Huang and M. Ismail, CMOS multiplier design using the differential difference amplifier, *Proc. IEEE Midwest Symp. Circuits Syst.*, 1993, pp. 1366–1368.
22. S. T. Lee, K. T. Lau, and L. Siek, Four-quadrant CMOS analogue multiplier for artificial neural networks, *Electron. Lett.*, **31**: 48–49, 1995.
23. S. Liu and Y. Hwang, CMOS four-quadrant multiplier using bias feedback techniques, *IEEE J. Solid-State Circuits*, **29**: 750–752, 1994.
24. C. Kim and S. Park, New four-quadrant CMOS analogue multiplier, *Electron. Lett.*, **23**: 1268–1270, 1987.
25. S. I. Liu, Low voltage CMOS four-quadrant multiplier, *Electron. Lett.*, **30**: 2125–2126, 1994.
26. Z. Wang, A four-transistor four-quadrant analog multiplier using MOS transistors operating in the saturation region, *IEEE Instrum. Meas.*, **42**: 75–77, 1993.
27. A. Diaz-Sánchez and J. Ramírez-Angulo, Design and implementation of VLSI analog adaptive filters, *Proc. IEEE Midwest Symp. Circuits Syst.*, 1996, pp. 1366–1368.
28. H. Song and C. Kim, An MOS four-quadrant analog multiplier using simple two-input squaring circuits with source followers, *IEEE J. Solid-State Circuits*, **25**: 841–848, 1990.
29. K. Kimura, Analysis of An MOS four-quadrant analog multiplier using simple two-input squaring circuits with source followers, *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, **41**: 72–75, 1994.
30. Y. Kim and S. Park, Four-quadrant CMOS analogue multiplier, *Electron. Lett.*, **28**: 649–650, 1992.
31. S. Sakurai and M. Ismail, High frequency wide range CMOS analog multiplier, *Electron. Lett.*, **28**: 2228–2229, 1992.
32. S. Liu and Y. Hwang, CMOS four-quadrant multiplier using bias offset cross coupled pairs, *Electron. Lett.*, **29**: 1737–1738, 1993.
33. S. Liu and Y. Hwang, CMOS squarer and four-quadrant multiplier, *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, **42**: 119–122, 1995.
34. S. Liu, C. Chang, and Y. Hwang, New CMOS four quadrant multiplier and squarer circuits, in *Analog Integrated Circuits and Signal Processing*, Boston: Kluwer Academic Publishers, 1996, Vol. 9, pp. 257–263.
35. J. Ramírez-Angulo, Highly linear four-quadrant analog BiCMOS multiplier for  $\pm 1.5V$  supply operation, *Electron. Lett.*, **28**: 1783–1784, 1992.
36. Z. Hong and H. Melchior, Four-quadrant CMOS analog multiplier, *Electron. Lett.*, **20**: 1015–1016, 1984.
37. H. R. Mehrvarz and C. Y. Kwok, A large-input-dynamic-range multi-input floating gate MOS four-quadrant analog multiplier, *Proc. IEEE Int. Solid-State Conf.*, pp. 60–61, 1995.
38. J. F. Schoeman and T. H. Joubert, Four quadrant analogue CMOS multiplier using capacitively coupled dual gate transistor, *Electron. Lett.*, **32**: 405–408, 1996.
39. Z. Hong and H. Melchior, Four-quadrant CMOS analog multiplier with resistors, *Electron. Lett.*, **21**: 531–532, 1985.
40. K. Bult and H. Wallinga, A CMOS four-quadrant analog multiplier, *IEEE J. Solid-State Circuits*, **SC-21**: 430–435, 1986.
41. P. J. Langlois, Comment on ‘A CMOS four-quadrant analog multiplier’: Effects of threshold voltage, *IEEE J. Solid-State Circuits*, **25**: 1595–1597, 1990.
42. J. Peña-Finol and J. A. Connelly, A MOS four-quadrant analog multiplier using the quarter-square technique, *IEEE J. Solid-State Circuits*, **SC-22**: 1064–1073, 1987.
43. N. Saxena and J. J. Clark, A four quadrant CMOS analog multiplier for analog neural networks, *IEEE J. Solid-State Circuits*, **29**: 746–749, 1994.
44. Z. Wang, A CMOS four-quadrant analog multiplier with single-ended voltage output and improved temperature performance, *IEEE J. Solid-State Circuits*, **26**: 1293–1301, 1991.
45. S. Liu and C. Chang, CMOS analog divider and four-quadrant multiplier using pool circuits, *IEEE J. Solid-State Circuits*, **30**: 1025–1029, 1995.
46. J. Remírez-Angulo, Yet another low-voltage four quadrant analog CMOS multiplier, *Proc. IEEE Midwest Symp. Circuits Syst.*, 1995.
47. K. Kimura, An MOS four-quadrant analog multiplier based on the multitail technique using a quadritail cell as a multiplier core, *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, **42**: 448–454, 1995.
48. M. Holler et al., An electrically trainable artificial neural network (ETANN) with 10240 floating gate synapses, *Proc. Int. J. Conf. Neural Netw.*, Washington, 1989, pp. 191–196.
49. S. Liu and C. Chang, CMOS subthreshold four quadrant multiplier based on unbalanced source coupled pairs, *Int. J. Electron.*, **78**: 327–332, 1995.
50. R. L. Aalke, S. F. Quigley, and P. W. Webb, Design of an analogue subthreshold multiplier suitable for implementing an artificial neural network, *IEEE Proc., Part G*, **139**(2): 261–264, 1992.
51. L. Song, M. I. Elmasry, and A. Vannelli, Analog neural network building blocks based on current mode subthreshold operation, *Proc. IEEE Int. Symp. Circuits Syst.*, 1993, Vol. 4, pp. 2462–2465.
52. D. Brodarac et al., Novel sampled-data MOS multiplier, *Electron. Lett.*, **18**: 229–230, 1982.
53. M. S. Piedade and A. Pinto, A new multiplier-divider circuit based on switched capacitor data converters, *Proc. IEEE Int. Symp. Circuits Syst.*, 1990, Vol. 3, pp. 2224–2227.
54. L. W. Messengill, A dynamic CMOS multiplier for analog neural network cells, *Proc. IEEE Custom Integr. Circuits Conf.*, 1990, pp. 26.4.1–26.4.4.
55. L. W. Messengill, A dynamic CMOS multiplier for analog VLSI based on exponential pulse decay modulation, *IEEE J. Solid-State Circuits*, **26**: 268–276, 1991.
56. B. A. De Cock, D. Maurissens, and J. Conelis, A CMOS pulse-width modulator/pulse-amplitude modulator for four-quadrant analog multipliers, *IEEE J. Solid-State Circuits*, **27**: 1289–1293, 1992.
57. D. M. W. Leenaerts, G. H. Joordens, and J. A. Hegt, A 3.3V 625kHz switched-current multiplier, *IEEE J. Solid-State Circuits*, **31**: 1340–1343, 1996.



58. U. Gatti, F. Maloberti, and G. Torelli, CMOS triode-transistor transconductor for high-frequency continuous-time filters, *Proc. IEE Circuits, Devices Syst.*, **141** (6): 462–468, 1994.
59. J. Ramirez-Angulo and E. Sánchez-Sinencio, Programmable BiCMOS transconductor for capacitor-transconductance filters, *Electron. Lett.*, **28**: 1185–1187, 1992.
60. K. Bult and G. J. G. M. Geelen, A fast settling CMOS op amp for SC circuits with 90-db DC gain, *IEEE J. Solid-State Circuits*, **25**: 1379–1384, 1990.
61. E. Sackinger and W. Guggenbuhl, A high-swing, high-impedance MOS cascode circuit, *IEEE J. Solid-State Circuits*, **25**: 289–298, 1990.
62. F. You et al., A design scheme to stabilize the active gain enhancement amplifier, *Proc. IEEE Int. Symp. Circuits Syst.*, 1995, pp. 1976–1979.

GUNHEE HAN  
Texas A&M University